Chapter 7

Lab 7 - Diode Applications

7.1 Objective

The objective of this lab is to introduce diodes and a few of their applications.

7.2 Materials

- Laptop with LTSpice
- Analog Discovery
- Breadboard
- Wiring kit
- Lab parts kit

7.3 Introduction

Diodes are a fundamental circuit element whose one-directional current flow has a variety of applications. Diodes can be used as indicators (light emitting diodes (LEDs)), voltage protection elements, and rectification.

7.3.1 Diode Operation

Each diode has an anode and cathode, Figure 7.1 (a), and conducts current one way once the voltage across the diode has reached the forward voltage, often called forward bias, VF ≈ 0.7 V. A diode can also conduct current in the opposite direction when the voltage across the diode is negative, often called reverse bias, where the breakdown voltage, VBR, is large, usually -50 V or less. There is often a small current that flows when a diode is reverse bias, but we will neglect that effect for the purposes of this lab. The schematic symbol for an LED is similar, Figure 7.1 (b), but indicates that light is generated when the diode is operating with a forward bias. And the I-V curve for a typical diode, Figure 7.1 (c).

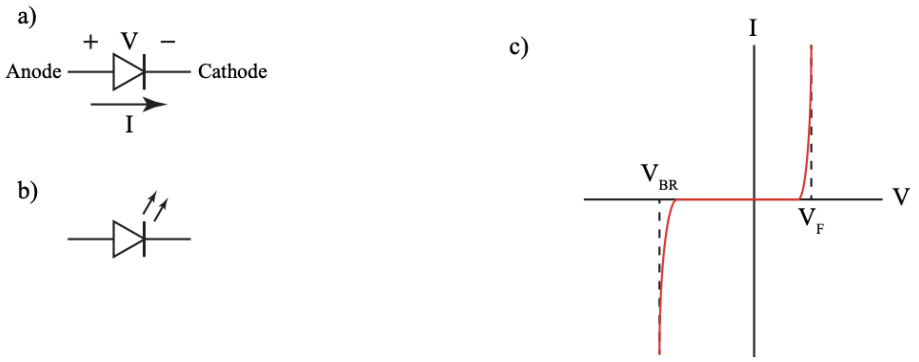


Figure 7.1: Diode schematic symbol with the anode and cathode labeled (a), schematic symbol for an LED (b), and the I-V curve for a diode (c).

7.3.2 Applications

There are a variety of applications for diodes and this lab will focus on only a few, rectifications, and clip detection.

Rectifiers

Half-wave Rectifier

Signal rectification is the process of converting an alternating signal in to its positive or negative components. Figure 7.2 is an example of a simple half-wave rectifier. After the input sine wave passes the diodes forward bias voltage, ≈ 0.7 V, the diode conducts and passes the positive half of the sine wave but doesn't pass the negative half of the sine wave because the diode is reverse bias and does not conduct.

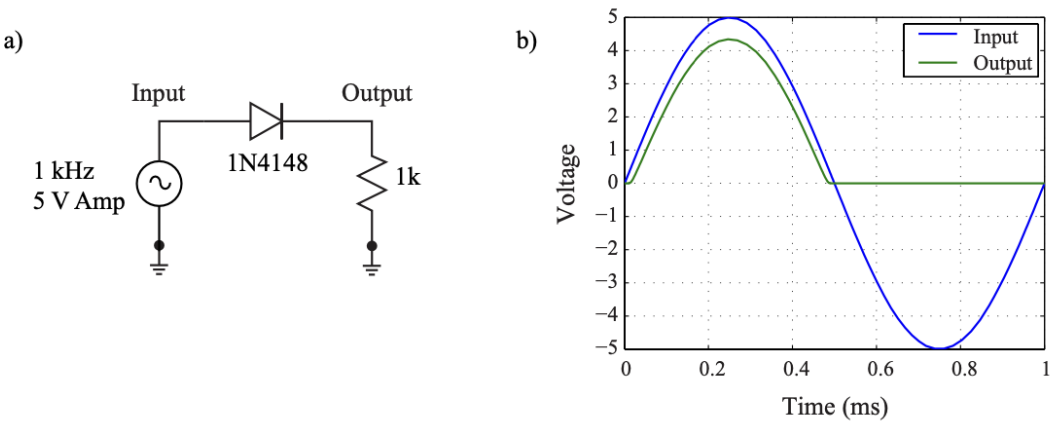


Figure 7.2: A simple half-wave rectifier (a) and the resulting input and output signals (b).

Simply adding a capacitor to the half-wave rectifier results in an AC to DC converter, Figure 7.3. The circuit initially behaves as it did previously, once the input sine wave reaches the forward bias voltage, the output follows the input. However, once the sine wave starts to decrease, the output then discharges as a function of an RC time constant, the process then repeats. For higher input frequencies and capacitances, the output cap be approximated as a DC source.

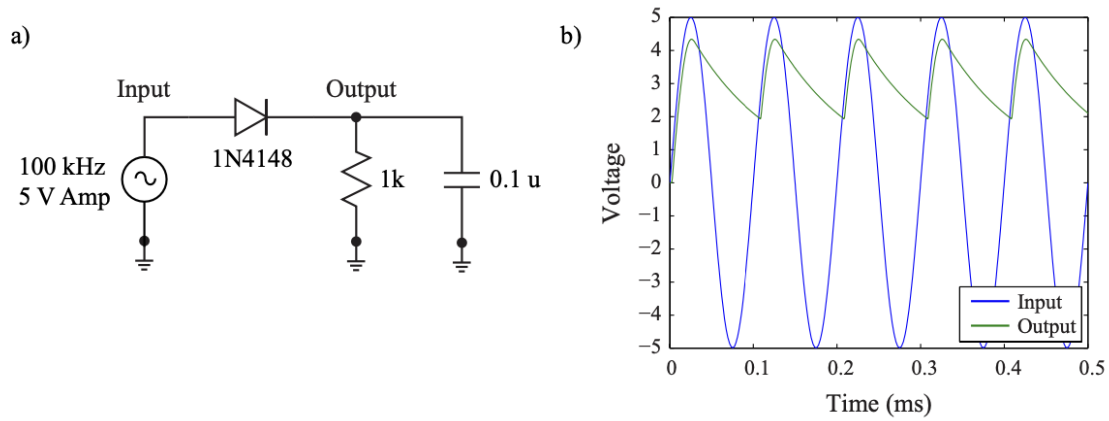


Figure 7.3: A simple half-wave rectifier but with a capacitor at the output (a) and the resulting input and output signals (b).

Full-Wave Rectifier

A full-wave (also called full-bridge) rectifier uses four diodes so that both halves of a sinusoidal input are routed to the load with the same polarity, producing a positive output for each half of the input. Because two diodes conduct in series on each half-cycle, the load voltage is reduced by about twice the diode forward drop. See Figure 7.4 for the schematic and waveforms.

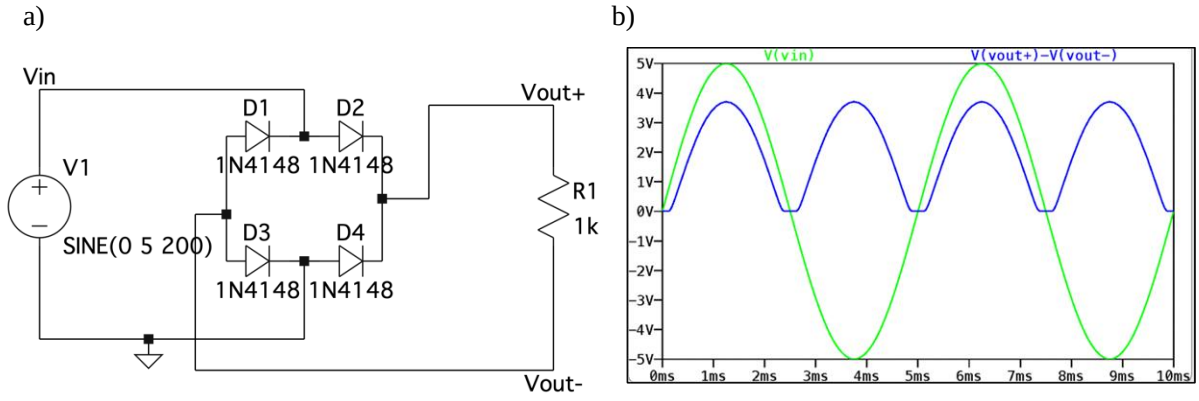


Figure 7.4: A full-bridge rectifier circuit (a) and it's resulting input and output signals (b).

Clip Detection

There are often cases where the input or output of a system isn't easily accessible for test equipment. A variety of dials, indicators, and display panels are often used to report on the status of a system, examples include current draw, internal voltages, and clip detection.

Clip detection is the process of determining if a signal is clipping or not. A signal that is clipped, unless desired, can degraded the performance of the system. A clipping detection circuit is able to indicate that the output of the op amp is clipping without viewing the output on an o-scope, but instead through an LED.

Figure 7.5 is an example of a clipping detector. If the input is higher, or lower, than the reference voltage VA, or VB, the LED D1, or D2, illuminates indicated that the input voltage is above, or below, the reference voltage. Note that this circuit does not use op amps, but comparators. Comparators, as the name implies, compares the input at both terminals and produces a digital output, either a 1 (5 V) or 0 (0V), if the positive terminal input is larger than the negative terminal input.

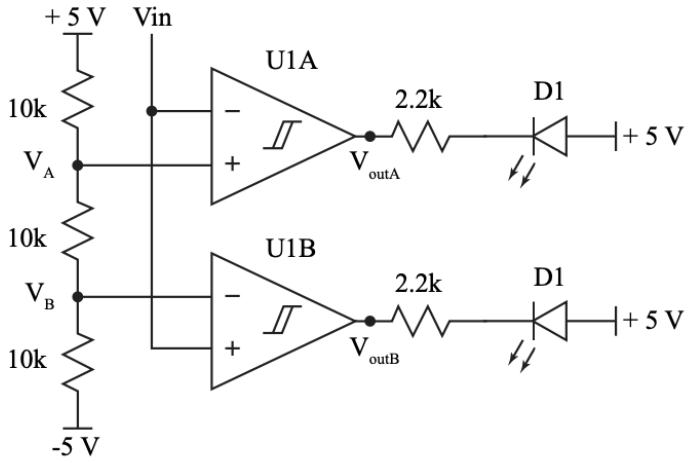


Figure 7.5: A clipping detection circuit. The input is compared to fixed voltages, V_A and V_B, by U1A and U1B respectively. If the input voltage is greater, or less, than the reference voltage, the output is pulled low and LED is illuminated.

7.3.3 Potentiometers

A potentiometer (or "pot") is a three terminal resistor as shown in Figure 7.6. The total resistance between terminals 1 and 3 is fixed and matches the potentiometer's rated value. Terminal 2 is connected to a sliding contact called the wiper, which moves along the resistive path inside. By adjusting the wiper, the resistance between terminals 2 and 1 or between 2 and 3 changes.

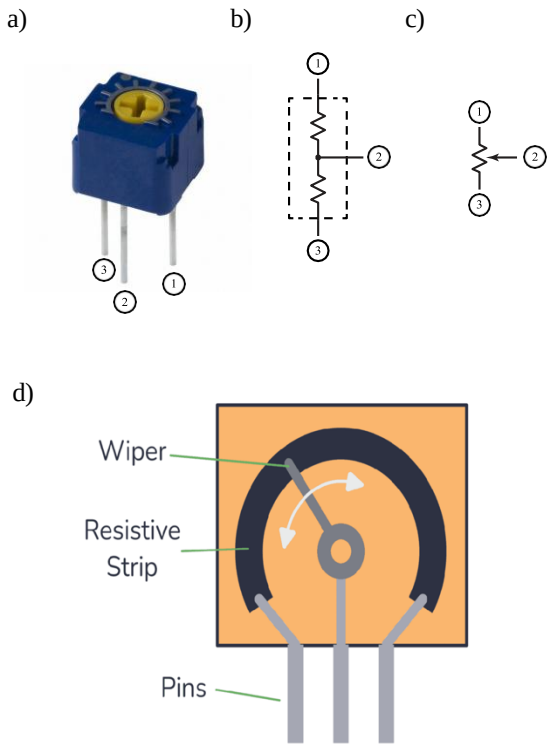


Figure 7.6: A picture of a practical potentiometer with the appropriate pins labeled (a), an equivalent circuit diagram of a potentiometer with the wiper in a fixed position (b), the common circuit schematic representation for a potentiometer (c), and a visual aid to help understand how the wiper adjusts the resistance (d).

To use a potentiometer on a breadboard, you can treat it like a standard two-terminal resistor by connecting only the center terminal (wiper) and one of the outer terminals. This allows the potentiometer to function as a variable resistor by adjusting the knob. The third unused pin can be left with no connection, do not try to bend it.

You can also use the potentiometer as a voltage divider. To do this, you would connect all three terminals: one outer terminal to Vcc, the other outer terminal to GND, and the center terminal becomes the adjustable voltage output.

In LTspice, a potentiometer is modeled using a resistor with a variable resistance. Instead of a dedicated component, you can define a resistor's value as {R_total * w}, where R_total is the max resistance (10k) and w (ranging from 0 to 1) represents the wiper position. For example, if you want the pot to be 5kΩ, the value of w would be 0.5 and the spice directive would be:

```
.param w=0.5
```

You can also calculate the resistance you need and just assign that value to the resistor in your schematic. To recall how variables work in LTspice, look back to the Monte Carlo simulations in Lab 2 where we define resistor tolerances.

7.4 Big Picture

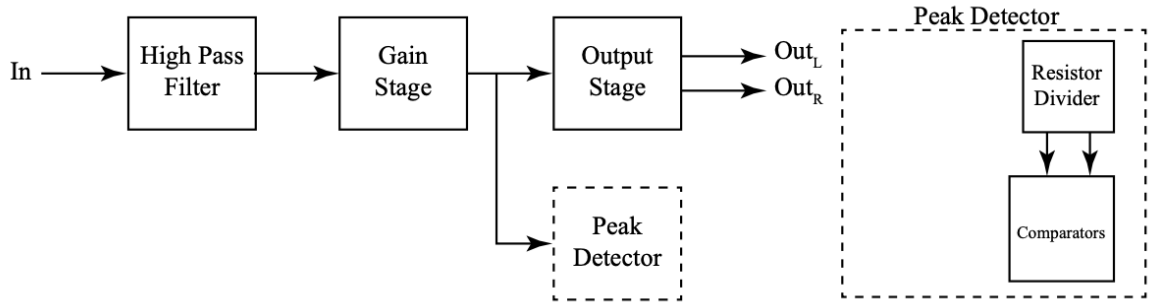


Figure 7.7: Big picture with emphasis on the peak detector.

This lab focuses on diode circuits which will help to form the comparator circuits used in the peak detector for the final project.

7.5 Pre-Lab Requirements

Complete the following before coming to lab.

7.5.1 LTspice Simulations

Using LTspice, complete the following.

1. Build the circuit in Figure 7.2 (a). Set the input to a 1 kHz, 5 V amplitude sine wave and run a transient simulation with a stop time of 1m (.tran 1m) and plot the input and output. To use the 1N4148 diode model, right click on the diode after placing it, Pick New Diode, and then choose the 1N4148 model (Mfg. OnSemi). Save an image of the circuit and the plot of the input and output voltage.

2. Build the circuit in , Figure 7.3 (a). Set the input to a 100 kHz, 5 V amplitude sine wave and run a transient simulation with a stop time of 50u (.tran 50u) and step through possible capacitor values using the following spice directive:

   ```
   .step param C list 0.001u 0.01u 0.1u 1u
   ```

   Save an image of the circuit and the plot of the input and output voltage.

3. Rebuild the circuit in Figure 7.4 (a) in LTspice and plot the input and output voltages. Use the 1N4148 diode and a sinusoidal input volage with 0 V offset, 5 V amplitude, and 200 Hz frequency. When plotting the output voltage, you must plot the difference between the two nodes of the load, just like in Figure 7.4 (b). Use .tran 10m for simulation. Take

screenshots of the schematic and voltage waveforms.

4. Build the circuit in Figure 7.5. Use the default LED model in LTSpice, and download "slcj016.zip" file from Lab 7 folder for the LM393 comparator model. Ensure the unzipped file ends correctly by opening it in a text editor. The final line should be "**.ENDS**" with no extra characters following it. If any exist, remove them, save the file, then proceed to import to LTspice.

   Import the model into LTspice using the "LTspice Component Import" documents in the lab folder. You can also find video instructions here. You don't need to adjust the component shape; it could lead to potential errors.

   Power the LM393 with ±5 V. Set the input voltage to a 1 kHz, 5 V amplitude sine wave and run a transient solution with a stop time of 2m (.tran 2m). Plot the input voltage and the current through each diode. Save an image of the circuit and the plot.

5. Build the circuit in Figure 7.8. Power the LM393 and TLV272 with ±5 V. Set the input voltage to a 1kHz, 0.1 V amplitude sine wave and run a transient solution with a stop time of 2m. Choose the value for R1, 10k pot, (vary the 'w' parameter or just hard code the value) so that the diodes conduct current and illuminate. Plot the input voltage, output of the op amp, positive and negative inputs to the comparator, and the current through both LEDs. (6 items total). Save an image of the circuit and the plots.

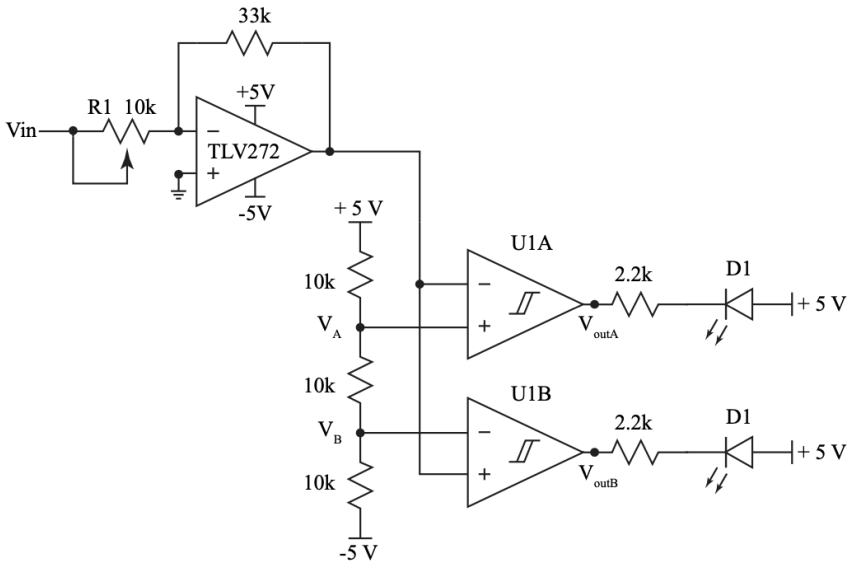


Figure 7.8: A variable gain amplifier, R1 is a potentiometer that can be varied, where the output is checked for clipping.

7.5.2 Breadboard Implementation

1. Read the datasheet for the LM393, the pinout for the chip is on page 3.

2. Build the circuit in Figure 7.5 on a breadboard. It is important to note that the pinout for the comparator chip is the same as the op amp. It works differently but should be connected the same as the op amp. This means you should still connect pin 8 to +5V and pin 4 to -5V (not GND) just as you have done with the op amp.

   Set the input to a 0.5 Hz, 5 V amplitude sine wave. Use the two red LEDS in your lab kit, they're bagged separately. The anode for the LEDs is the longer of the two leads. The diodes will illuminate whenever the input voltage is above or below the reference voltage and should appear to blink in turn. Save the circuit to show your lab instructor at the start of lab.

7.5.3 Pre-Lab Checklist

The following must be completed at the start of lab.

1. Section 8.5.1

   (a) Item 1: Half-wave rectifier, image of the circuit and the plot of the input and output voltage.

   (b) Item 2: Half-wave rectifier with output smoothing, image of the circuit and the plot of the input and output voltage.

   (c) Item 3: Full-wave rectifier, image of the circuit and plot of the input and output voltage.

   (d) Item 4: Clipping circuit, image of the circuit and the plot.

   (e) Item 5: Variable gain amplifier with clip detector, image of the circuit and the plot.

2. Section 8.5.2

   (a) Item 2: Operational clipping circuit demo.

7.5.4 Breadboard Implementation

1. Plot the input voltage and the voltage at the output of either comparator, Figure 7.5, on the o-scope and save an image of the display.

2. Build the circuit from Section 8.5.1 - Item 1. Plot the input and output on the o-scope and save an image of the display.

3. Build two versions of the circuit from Subsection 8.5.1 - Item 2, one with where the

capacitance is 0.1 uF and the other is 0.01 uF. Plot the outputs of both circuits on the o-scope and save an image of the display.

4. Implement the full-bridge circuit from Subsection 8.5.1 - Item 3. Set Wavegen 1 to a 200 Hz, 5 V amplitude sine wave. When measuring the output, connect Scope 2+ to Vout+ and Scope 2- to Vout- to get the differential signal. Plot the outputs of both circuits on the o-scope and save an image of the display.

5. Build the circuit from Subsection 8.5.1 - Item 5. Set the input to a 0.5 Hz, 0.1 V amplitude sine wave. Vary the potentiometer, increase the gain, so that the LEDs illuminate when the op amp output is greater than the reference voltages. Plot the output of the gain amplifier and the output of either comparator on the o-scope and save an image of the display.

7.6 Write Up

Discuss the functionality and operation of each circuit built in lab, include your captured waveforms and corresponding LTspice schematics. By this point, you have worked with both op amps and comparators. Compare their similarities and differences. When would you choose an op amp over a comparator, and vice versa, based on application?

Refer back to the clipping detection circuit in Figure 7.5. For the final project, you will be asked to design a circuit where one LED turns on when the input voltage exceeds 1 V and the other LED turns on when the input voltage exceeds 4 V to indicate clipping. Calculate the resistor values needed to set the correct reference voltages using either ± 5 V supply or +5 V and GND supply for the three-resistor ladder. You do not need to get exactly 1 V and 4 V, get as close as you can only using 3 resistors. Explain your reasoning.